 


# **COMP2611: Computer Organization**


## **Introduction to Digital Logic**
 
### **Sequential Logic**


- ❑ Till now, we have essentially ignored the issue of time. We assume digital circuits:
  - ❑ Perform their computations instantaneously
  - ❑ Stateless: once you present a new input, they forget everything about previous inputs
- ❑ In reality, time is an important issue:
  - ❑ Logic gate induces a small amount of delay (on the order of a few nanoseconds)
  - ❑ We want our circuit to have some form of memory



- ❑ A microprocessor is composed of many different circuits that are operating simultaneously – if each circuit  $X$  takes in inputs at time  $T_{in}$ , takes time  $T_{exe}$  to execute the logic, and produces outputs at time  $T_{out}$ , imagine the complications in coordinating the tasks of every circuit
- ❑ Solution: all circuits on the chip share a clock signal (a square wave) that tells every circuit when to accept inputs, how much time they have to execute the logic, and when they must produce outputs




 
- ❑ A **clock** is a free-running signal with a fixed **cycle time** (called **clock period**) or, equivalently, a fixed **clock frequency** (i.e., inverse of the cycle time).
- ❑ **Edge-triggered clocking:**
  - ❑ Design methodology for sequential logic circuits in which all state changes occur on a clock edge (**rising edge** or **falling edge**).




- ❑ Example  $4 \text{ GHz} = \text{clock speed} = \frac{1}{\text{cycle time}} = \frac{1}{250 \text{ ps}}$

 - ❑ Clocked systems are also called **synchronous systems**.
- ❑ **Sequential logic circuits** are circuits whose output depends on **both** the current input and the value stored in the memory of the circuit (called **state**)
- ❑ Sequential logic circuits often depend on a clock to determine when the memory or state element of the circuit is updated.



 

Combinational

 


Sequential

- ❑ Consists of combinational circuit and a storage elements
- ❑ The rising/falling edge causes the 'state' storage to store some updated values
- ❑ This state will not change for an entire cycle (until next rising/falling edge)
- ❑ The combinational circuit has some time to accept the value of 'state' and 'inputs' and produce 'outputs'
- ❑ Some of the outputs (i.e. the value of the next 'state') may feed back and they're only seen in the next cycle
- ❑ Example: counter, register

❑ **S-R latches** (set-reset latches):

 - ❑ **Unclocked** memory element built from a pair of cross-coupled NOR gates (i.e., OR gates with inverted outputs).




Inputs		Outputs	
R	S	Q	Not Q
0	0	Latch	
1	0	0	1
0	1	1	0
1	1	Invalid Input	

❑ **Operation:**

- When Set is **asserted** (high), a 1 is stored
- When Reset is asserted, a 0 is stored
- When both are **de-asserted** (low), the previous state is preserved
- When both are high, the output is unstable,- this set of input is therefore not allowed

 - ❑ **D latches** are **clocked** (i.e., state changes are triggered by a clock).
- ❑ **Operation:**
  - ❑ the value of the input D signal (data) is stored only when the clock signal C is asserted – the previous state is preserved when the clock is de-asserted.




Inputs		Outputs	
C	D	Q	Not Q
0	0	Latch	
0	1	Latch	
1	0	0	1
1	1	1	0




## ❑ Digital timing diagram

- ❑ A representation of a set of signals in the time domain
- ❑ Can contain many rows, usually one of them being the clock


 
## ❑ **Example:** timing diagram of D latch



 - ❑ **D flip-flops**, like D latches, are **clocked**.
- ❑ **Terminology:**
  - ❑ Latch: outputs can change any time the clock is asserted (high)
  - ❑ Flip-flop: outputs can change only on a clock edge
- ❑ **Falling-edge-triggered master-slave D flip-flop:**
- ❑ Operation:
  - ❑ When the clock input C changes from asserted to de-asserted, the Q output stores the value of the D input.




- D-Latches and flip-flops can be used to build memory elements used by digital computers to hold data temporarily.
- **register file** is a structure in the datapath consisting of a set of registers that can be read and written by supplying a register number to be accessed. These represent the hardware “variables”
- **Static random access memories (SRAMs)**: relatively small memories used for cache and built with flip-flops

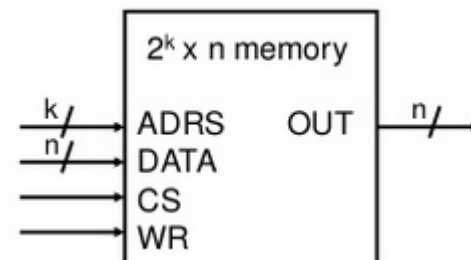 

Block diagram of RAM chip
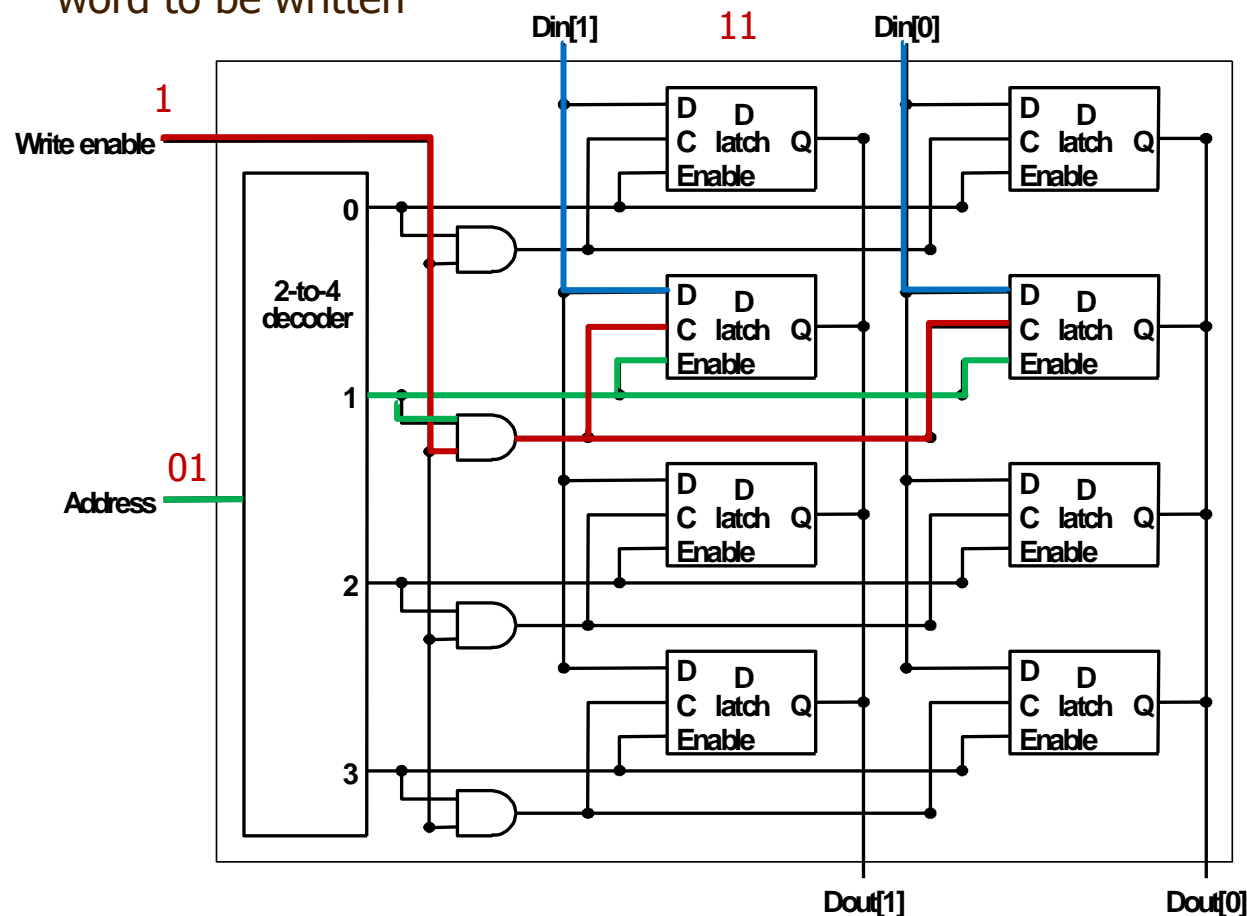
## ❑ Operation

- ❑ Stores 4 words of data each word has 2 bits
- ❑ Reads the content of one word at a time by supplying its address on 2 bits (i.e., word 00, or 01, or 10, or 11)
- ❑ Write data to one word by supplying 2 bits of Data and the 2-bit address of the word to be written



- ❑ Computers use two reference levels of voltage to represent data as binary digits
- ❑ **Boolean Algebra** to express any operation on bits as a logic equation or a equivalently a truth table
  - ❑ Three basic operations: AND, OR, and NOT
  - ❑ Basic rules of Boolean Algebra
- ❑ **The transistor (an electronic switch)** is the basis for building logic gates
- ❑ **Logic Gates** are basic building blocks of more complex logic circuits

- ❑ Two types of logic circuits:
  - ❑ **Combinational circuits**: process the inputs to produce the output
    - Multiplexers
    - Decoders
    - Arithmetic and logic operations
  - ❑ **Sequential circuits**: process the input and the **state element** (memory) of the circuit to produce the output
    - Memory, registers
    - Not possible to access (read) and update (write) the state element simultaneously, therefore a clock is necessary to control when operations are done
    - **Edge-triggered clocks** are more efficient and more accurate, than level-based clocks
    - Latches, Flip-flops